

Experiment - 2

Aim: Verification of KVL and KCL using given circuit.

Requirement: Multisim live ([www.multisim.com](http://www.multisim.com)).

Apparatus :-

S.No	Apparatus	Specification	Quantity
1	Multimeter	Digital	01
2	Power supply	DC Regulated	01
3	Bread Board	-	01



Components Required :-

S.No.	Apparatus	Specification	Quantity
1	Resistors	1 k $\Omega$	02
2	Resistors	4.7 k $\Omega$	01

Theory

There are two Kirchhoff's laws

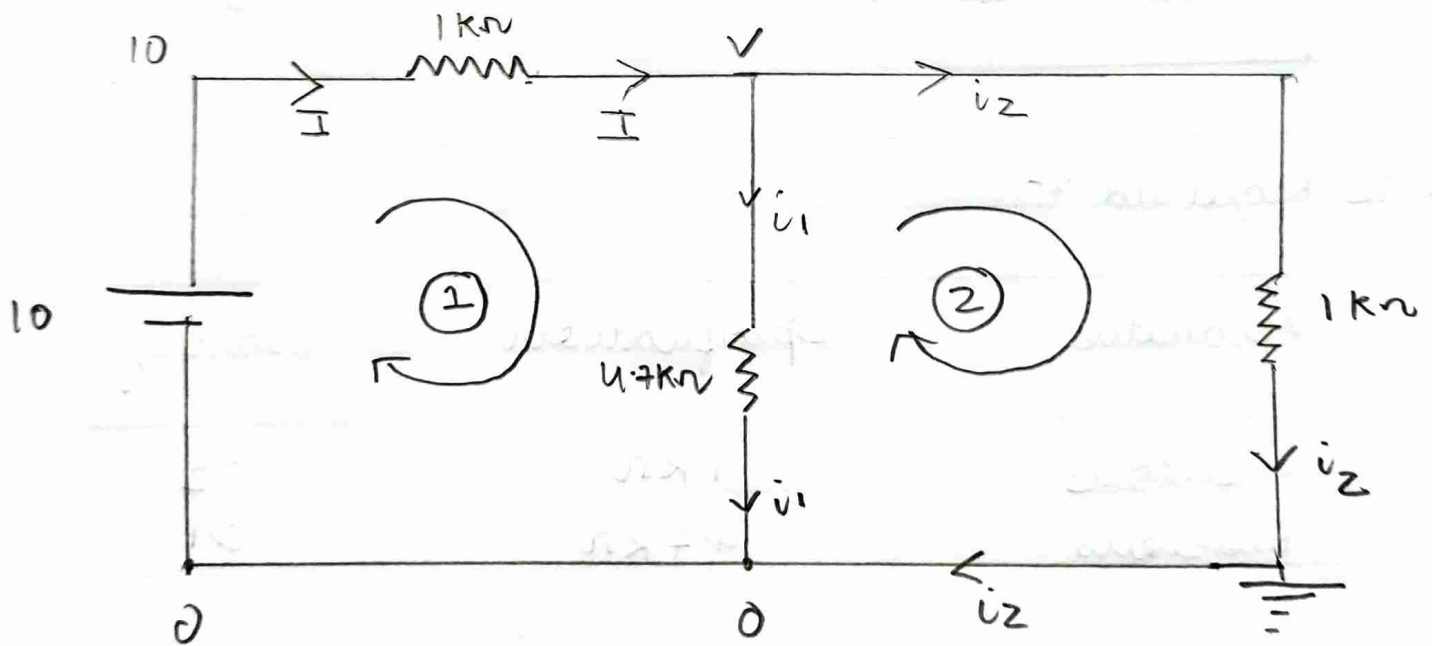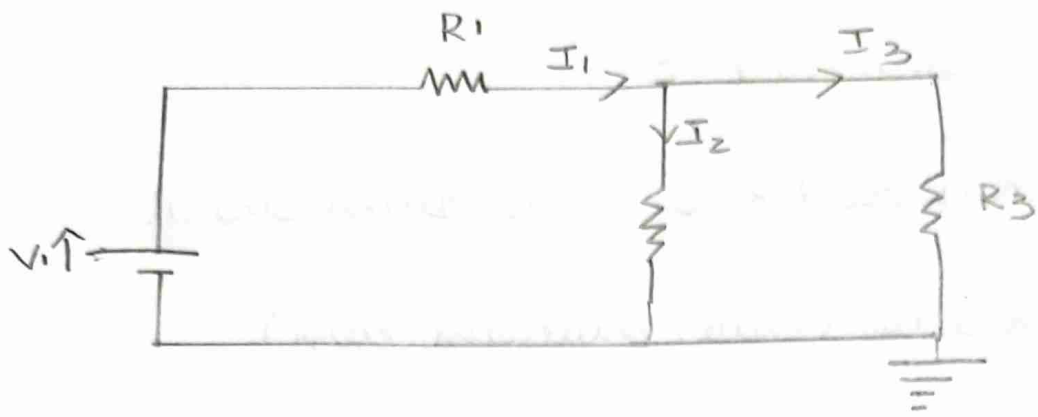- (a) Kirchhoff's Voltage Law (KVL)
- (b) Kirchhoff's Current Law (KCL)



- KVL states that the algebraic sum of all the voltages encountered as one goes around in complete loop is zero.
- (KCL) Kirchhoff's current law states that the algebraic sum of all the currents entering or leaving a junction or node is zero.

## Observation Table

Input Voltage	$V(R_1)$	$V(R_2)$	$V(R_3)$	$I(R_1)$	$I(R_2)$	$I(R_3)$
10	5.4808	4.5192	4.5192	5.4808	<del>961.54</del> 961.54	4.5192
	volts	(V)	(V)	(mA)	(mA)	(mA)

## KVL loop ①

$$10 - I_1 - i_1 \times 4.7 = 0$$

$$I = I_1 + I_2$$

$$10 - 5.7i_1 - i_2 = 0 \Rightarrow \text{①}$$

loop ②

$$4.7i_1 - i_2 \times 1 = 0$$

$$i_2 = 4.7i_1 - \text{②}$$

From ② and ①

$$10 - 4i_1 = 10$$

$$i_1 = 10$$

$$10.4 \text{ k}\Omega$$

$$i_1 = 961.54 \text{ mA}$$

from ②

$$i_2 = 4.7 i_1$$

$$i_2 = 4519.238 \mu A$$

K.C.L (Summation of currents through nodes is '0')

$$\frac{10-V}{1K} + \frac{0-V}{1K} + \frac{0-V}{4.7K} = 0$$

$$\frac{1}{K} \left( \frac{47 - 4.7V - 4.7V - V}{4.7} \right) = 0$$

$$47 = 9.4V + V$$

$$47 = 10.4V$$

$$V = 4.5192V$$

Result: Hence KVL and KCL are verified.

Precaution: Circuit must be grounded.

Learning outcomes:-

1. The sum of all currents entering a junction must be equal to the sum of all currents leaving junction.
2. The algebraic sum of all the voltage around any closed loop in a circuit is equal to zero.



